

6234
BOARD DIPLOMA EXAMINATION
JUNE - 2019 DIPLOMA IN DIPLOMA IN COMPUTER ENGINEERING

*

DIGITAL ELECTRONICS
THIRD SEMESTER EXAMINATION

Time: 3 Hours

Total Marks: 80

PART - A (3m x 10 = 30m)

Note 1: Answer all questions and each question carries 3 marks

2: Answers should be brief and straight to the point and shall not exceed 5 simple sentences

1.

Find the 1's complement to the following numbers

2. i) **1010112** and ii) **1110112**

Convert the following binary numbers into Grey code

3. i) **111102** and ii) **100102**

Define the following terms related to logic families

4. i **Propagation Delay** ii) **Noise margin** iii) **Fan-out**

Compare the performance of serial adder and parallel adder with respect to following parameters

5. i) **No. of Full adders** and ii) **Need of delay circuit**

6. **Draw the logic circuit of two bit digital comparator**

7. **State the need for Preset and clear inputs**8.

List commonly used IC numbers of Flip-flops and counters

*

9. **Distinguish between Edge Triggering and Level Clocking**10.

Draw the diagram of shift left register

PART - B (10m x 5 = 50m)

Note 1: Answer any five questions and each carries 10 marks

2: The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer

11.

Obtain the Logic expression for the output Y and simplify for the given logic diagram

$$Y = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

*

www.manareresults.co.in

Page: 1 of 2

Code: C16 EC-303

12.

| A | B | OUTPUT |
|---|---|--------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

a) Classify different Logic Families

b) Define the following terms related to logic families

13. i) Propagation Delay ii) Noise margin iii) Fan-in

a) Draw the Half adder using NAND gates

14. b) Illustrate the concept of combinational logic circuits

a) Draw the working of BCD to Decimal Decoder

b) Explain the working of BCD to Decimal decoder using above logic

15. diagram

a) Explain the race-around condition

b) Explain the function of clocked D flip-flop using above diagram

16. and truth table

17. Explain the working of 4-bit Ring counter

a) Draw the 4-bit shift left register, truth table and its timing diagram

b) Explain the function 4-bit shift left register with help of above

18. diagram

- XXX -

*

*

www.manareresults.co.in

Page: 2 of 2