



6 2 3 4

\*

C16-CM-303

**6234**

**BOARD DIPLOMA EXAMINATION, (C-16)**

**MARCH/APRIL—2021**

**DCME - THIRD SEMESTER EXAMINATION**

**DIGITAL ELECTRONICS**

*Time : 3 hours ]*

*[ Total Marks : 80*

---

**PART—A**

**Instructions :** (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Convert decimal number 124.6 into Binary and Hexadecimal.  $1\frac{1}{2}+1\frac{1}{2}$

2. Subtract 101010 from 110111 using 2's complement method. 3

3. Write the Excess-3 code and Gray code for decimal digit 9.  $1\frac{1}{2}+1\frac{1}{2}$

4. Define propagation delay and fan-out of digital ICs.  $1\frac{1}{2}+1\frac{1}{2}$

5. List the applications of multiplexer. 3

6. Draw the logic circuit of half adder using NOR gates only. 3

7. Differentiate between level clocking and edge triggering. 3

8. Draw NOR latch with truth table. 3

9. List the applications of flip-flops. 3

10. Write differences between EEPROM and UVEPROM. 3

www.manareresults.co.in

\*

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

**11.** (a) Explain working of AND, NOR and EX-OR gates with truth

(b) Minimize  $\bar{A}BC + \bar{A}BC + ABC + ABC$  using Karnaugh map. 4

**12.** (a) State De-Morgan's theorems. 4

(b) Realize AND, OR and NOT gates using NOR gates. 6

**13.** Explain the working of open collector TTL NAND gate with circuit diagram. 10

**14.** Explain the working of 2's complement adder/subtractor with logic block diagram. 10

**15.** Draw and explain the working of decimal to BCD encoder. 10

**16.** Draw and explain the working of asynchronous decade counter. 7

**17.** (a) Draw and explain the working of 4-bit ring counter. 3

(b) Draw the logic circuit of 3-bit asynchronous up-down counter.

**18.** Draw and explain the working of 4-bit shift right register with timing

diagram.

10  
-- - -

★ ★ ★

/6234 \*

2

AA21-PDF  
6

tables.

[www.manareresults.co.in](http://www.manareresults.co.in)